

0, 1, 2, 3, 4, 5, 6

0, 6, 5, 4, 3, 2, 1

Current State			Next state		
	$e=0$		$e=1$		
A	0	000	A	B	001
B	1	001	B	C	010
C	2	010	C	D	011
D	3	011	D	E	100
E	4	100	E	F	101
F	5	101	F	G	110
G	6	110	G	A	000
H	7	111	H	A	000

$e = \text{on/off}$      $u = \text{up/down}$

$G_1, G_2$

$G_1, G_2$

	00	01	11	10
00	000	001	011	010
01	100	101	111	110
11	100	101	111	110
10	000	001	011	010

	00	01	11	10
00	110	000	010	001
01	011	100	110	101
11	101	110	000	000
10	001	010	100	011

$e=0$

$e=1$

J

	00	01	11	10
00	0	0	0	0
01	X	X	X	X
11	X	X	X	X
10	0	0	0	0

J

	00	01	11	10
00	1	0	0	0
01	X	0	X	X
11	X	X	0	X
10	0	0	1	0

JK

	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$G_1, G_2$

$G_1, G_2$

	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

	00	01	11	10
00	1	0	0	0
01	0	1	1	1
11	1	1	0	0
10	0	0	1	0

$e=0$

$e=1$

$e=0$

$e=1$

$$J_1 = e\bar{u}\bar{G}_1\bar{G}_2 + euG_1G_2$$

$$e(\bar{u} \oplus \bar{G}_1 \oplus \bar{G}_2)$$

$$K_1 = e\bar{u}\bar{G}_1\bar{G}_2 + euG_1$$

J

	00	01	11	10
00	0	0	X	X
01	0	0	X	X
11	0	0	X	X
10	0	0	X	X

J

	00	01	11	10
00	1	0	X	X
01	1	0	X	X
11	0	1	X	X
10	0	1	X	X

JK

	00	01	11	10
0	0	0	1	1
1	1	0	0	1

X

	00	01	11	10
00	X	X	0	0
01	X	X	0	0
11	X	X	0	0
10	X	X	0	0

X

	00	01	11	10
00	X	X	0	1
01	X	X	0	1
11	X	X	1	1
10	X	X	1	0

$G_1, G_2$

	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$G_1, G_2$

	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	0	1	0	0
10	0	1	0	1

$e=0$

$e=1$

$$J_2 = e \bar{u} \bar{G}_2 + e u G_2 = e (\bar{u} \oplus G_2)$$

$$K_2 = e (\bar{u} \bar{G}_2 + u G_0 + u G_2) = e (u G_0 + (\bar{u} \oplus G_2))$$

D

	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

D

	00	01	11	10
00	0	0	0	1
01	1	0	0	1
11	1	0	0	0
10	1	0	0	1

$e=0$

$e=1$

D

	0	1
0	0	1
1	0	1

$G_1, G_2$

	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0

$G_1, G_2$

	00	01	11	10
00	0	0	0	1
01	1	0	0	1
11	1	0	0	0
10	1	0	0	1

$e=0$

$e=1$

$$D_3 = \bar{e} G_2 + e (\bar{u} G_1 \bar{G}_2 + G_0 \bar{e} \bar{G}_2 + u \bar{G}_0 \bar{G}_2)$$

$$= \bar{e} G_2 + e \bar{G}_2 (\bar{u} G_1 + G_0 \bar{G}_1 + u \bar{G}_0)$$